

Impedance & Audio Interfaces

PNW Chapter of the AES
March 2017


Electrical Impedance Basics

Resistance (Resistor)

Ratio of current (I) and voltage (E or V)

Unit: Ω , Ohm

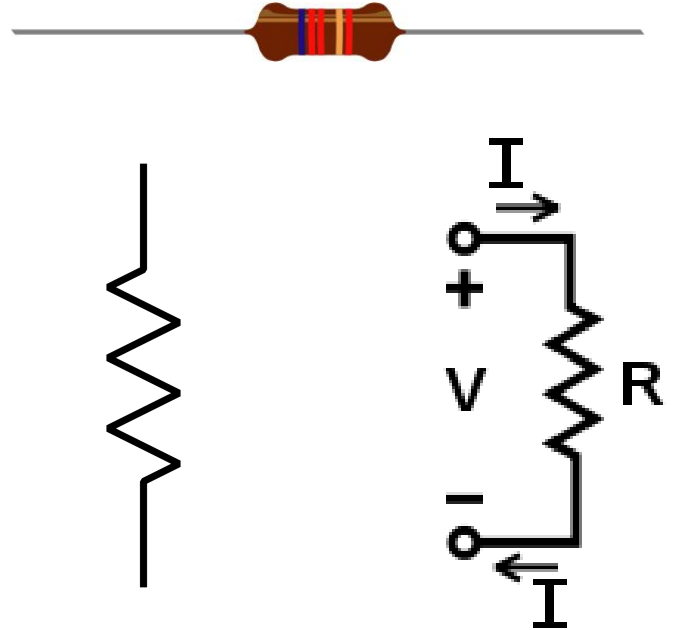- Resistors
- Wires
- Circuit board traces



Electrical Impedance Basics


Capacitive Reactance (Capacitor)

Ratio of current (I) and the *change in voltage over time* (dV/dt)

Units: F, Farads

- Capacitors
- Two wires near each other
- PCB Traces near each other
- Any two conductive surfaces

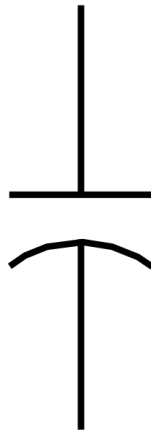“Resists” instantaneous changes in voltage




Electrical Impedance Basics

Inductive Reactance (Inductor)

Ratio of voltage (E or V) and the *change in current over time* (di/dt)

Units: H, Henries

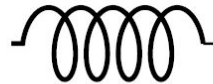- Inductors
- Wires or coils of wire
- PCB Traces
- Transformers



“Resists” instantaneous changes in current

Audio Interfaces

What's the point of connecting two things together?

- Information transfer
- Information in what form?
 - Analog audio: frequency, phase and amplitude
 - Digital audio: frequency (data rate)
 - **The higher the frequency, the more cable / wire impedance matters**
- Across what distance?
 - **The longer the distance, the more cable / wire impedance matters**

Audio Interfaces


What to do with this information?

- Measure it (microphone level or line level audio)
 - Transfer a measureable voltage
 - Minimizes losses in the interface
- Do some work with it (telephone system or power amplifier)
 - Transfer usable power
 - Drive a loudspeaker
 - Heat a rack room
 - More losses in the interface
- Go the distance
 - Transmission line behaviors

Audio Interfaces: Voltage Transfer

Very common in pro and consumer audio systems

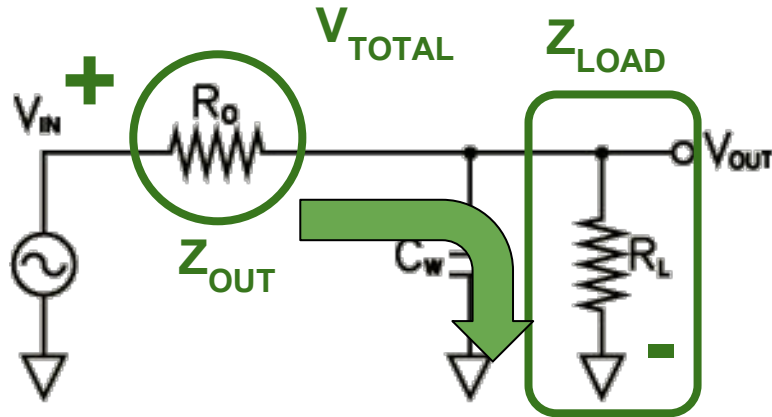Voltage divider when reactance is minimized



For 500 ft Belden 8451,
 $C_W = (34 \text{ pF/ft})(500 \text{ ft}) = .017 \mu\text{F}$

(1) Bohn / Rane

Resistive Voltage Divider:

$$R_L > 10 * R_O$$


$$\begin{aligned} V_{OUT} &= V_{IN} * (R_L / (R_O + R_L)) \\ &= V_{IN} * (10 / 11) \end{aligned}$$

$$V_{OUT} = 90.9\% \text{ of } V_{IN}$$

Audio Interfaces: Cable Capacitance

Cable specs typically note the capacitance per unit length in picofarads (pF)

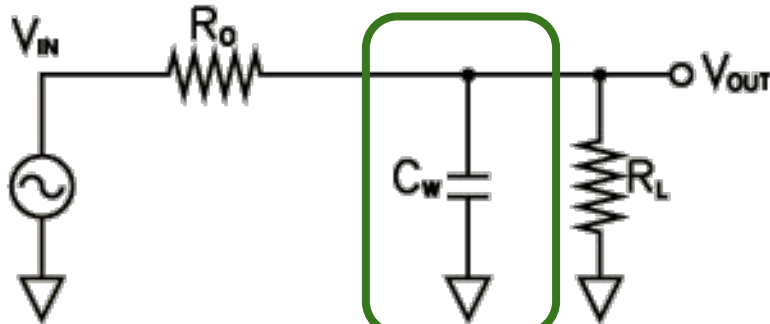At higher frequencies the cable impedance increases, lowering signal level



For 500 ft Belden 8451,

$$C_W = (34 \text{ pF/ft})(500 \text{ ft}) = .017 \mu\text{F}$$

(1) Bohn / Rane

RC Low pass filter

$$f_c = 1/(2\pi * R_O * C_W)$$

$$R_O = 200 \text{ ohms}$$

$$C_W = 0.017 \mu\text{F}$$


$$f_c = 1/(2\pi * 200 * 0.017 * 10^{-6})$$

$$f_c(-3 \text{ dB down}) = 46.8 \text{ kHz}$$

Audio Interfaces: Balanced Impedance

“In a balanced interconnect system both of the signal conductors have an equal, and nonzero, impedance to ground.” (2)

(Henry Ott consultants)

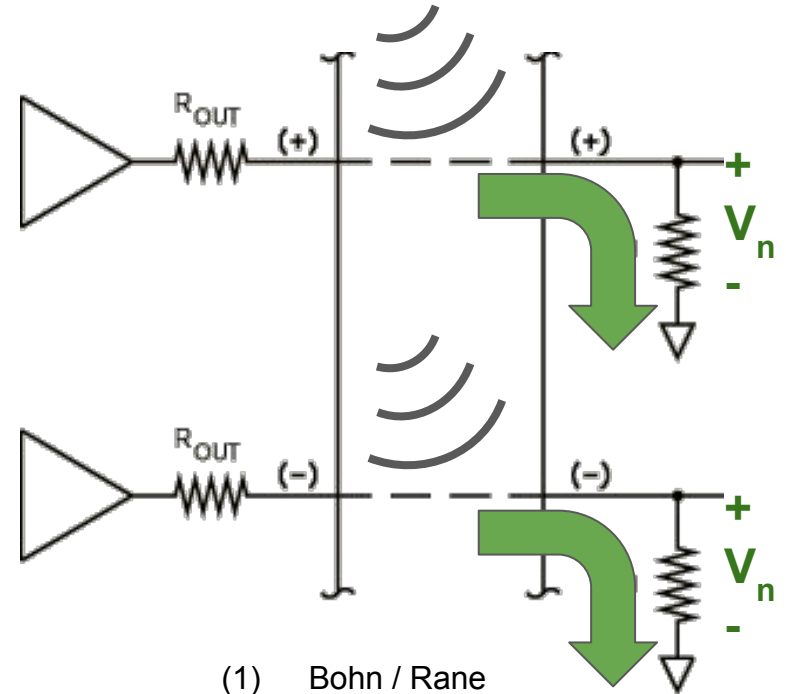

Audio Interfaces: Power Transfer


Electrical Power:

$$P = V * I \quad (\text{or historically... } P = E * I)$$

Unit: Watts (Joules per second)

When is power necessary?

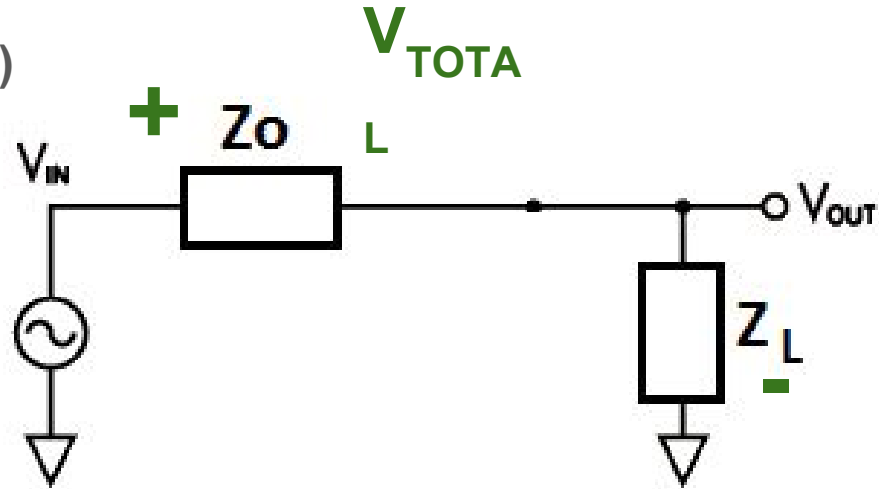- **Do some work**
 - Move air using a loudspeaker
 - Turn a crank



(1) Bohn / Rane

Audio Interfaces: Power Transfer


Interface Power:

$$I_{\text{TOTAL}} = V_{\text{TOTAL}} / (Z_{\text{TOTAL}})$$

$$P = I_{\text{TOTAL}} * (V_{\text{TOTAL}})$$


$$P = V_{\text{TOTAL}}^2 / Z_{\text{TOTAL}}$$

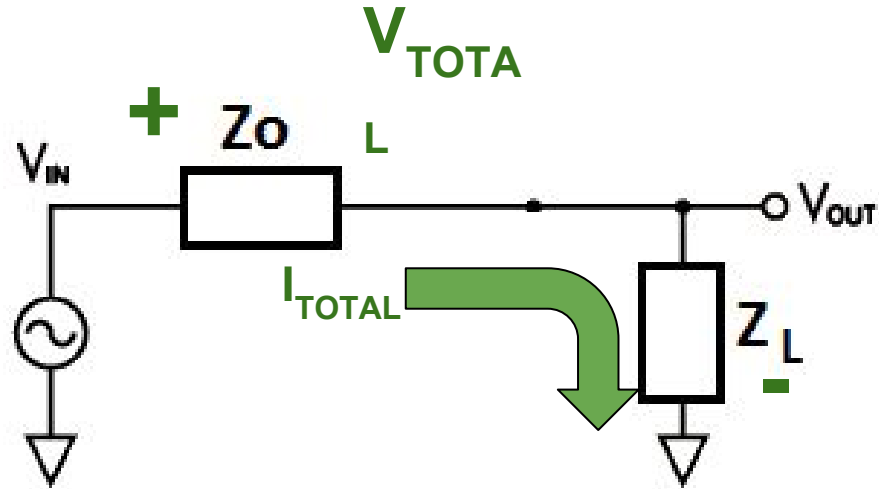- For fixed max voltage, interface power is determined by input and output impedance



(1) Bohn / Rane

Power Transfer: Impedance Matching

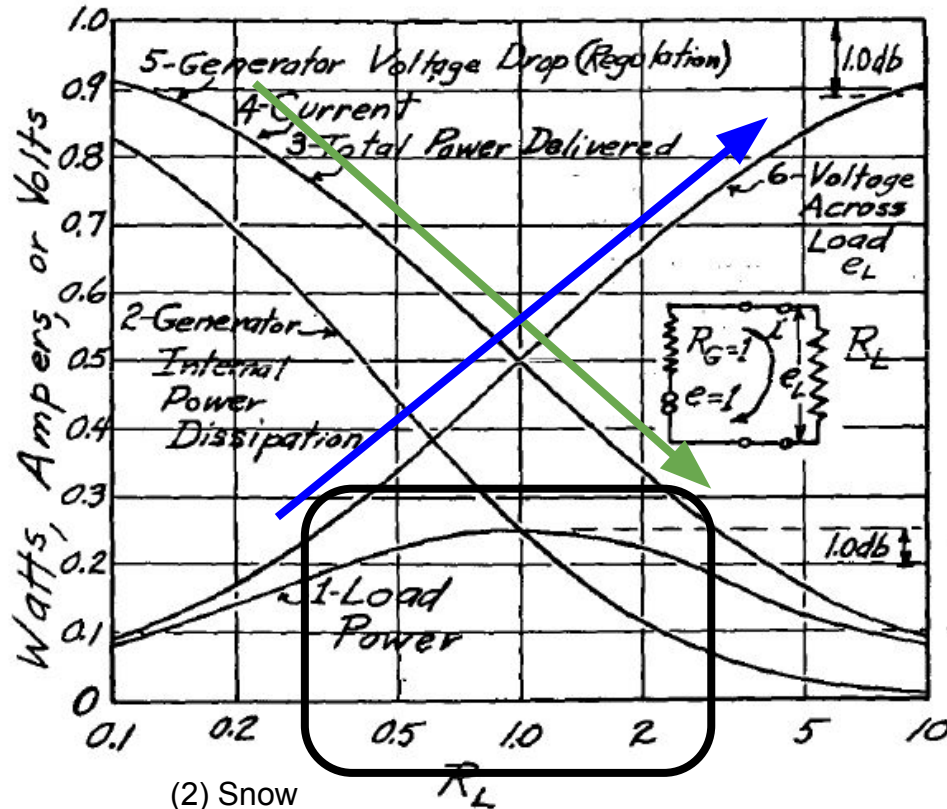

Example:

Tube amplifier output transformers




- $Z_{OUT} \sim 2 \text{ k}\Omega$, $Z_L \sim 8 \Omega$
- Transformer turns ratio matches low- z loudspeaker impedance to high- Z amplifier output impedance

Transmission Lines

- When cable lengths exceed one wavelength of the highest frequency, transmission line behaviors must be addressed
- Source and load termination is recommended when lines approach $\frac{1}{4}$ wavelength

$\frac{1}{4}$ Wavelengths:


- 20 kHz - 3.75 km
- 6.144 MHz - 12.2 m

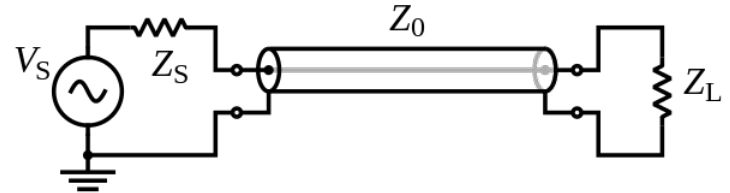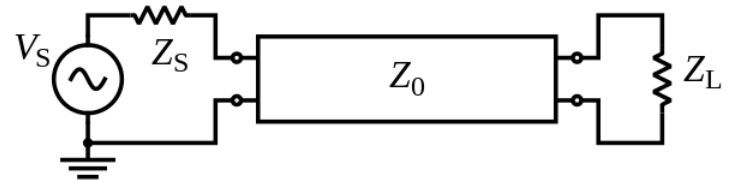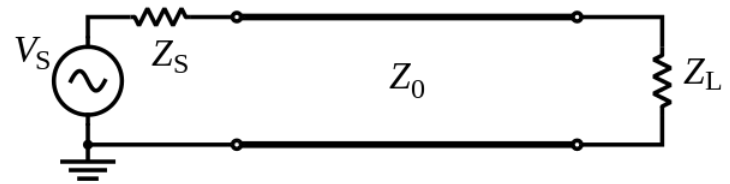

Transmission Lines: Wave Propagation



Transmission Lines: Impedance Matching

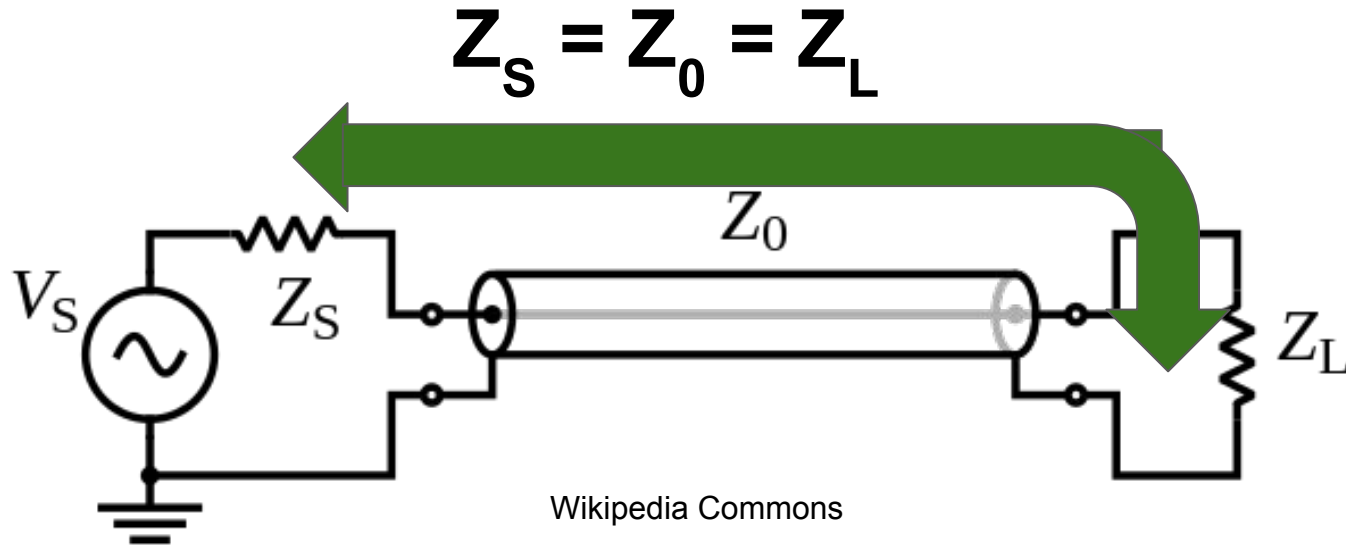


- Without proper termination, reflections will continue until dissipated
- Every out of phase reflection can cause destructive interference

Telephone Transmission Lines



University of California

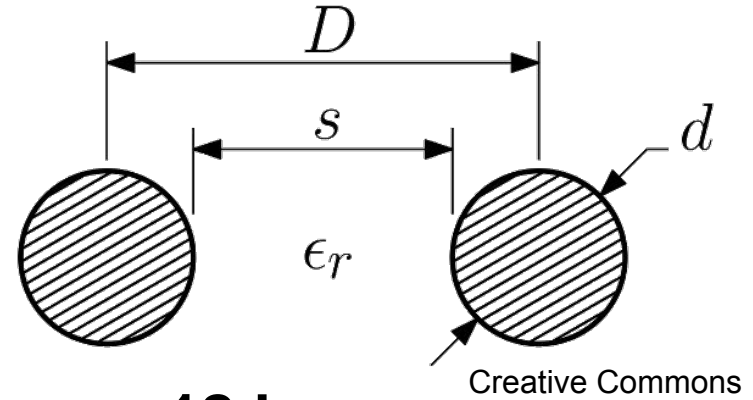


$$s = 12 \text{ in.}$$

$$\epsilon_r = 1.0054 \text{ (air)}$$

$$d = 0.1620 \text{ in. (6 AWG)}$$

$$Z_0 = 598.2$$

AES/EBU Transmission Lines

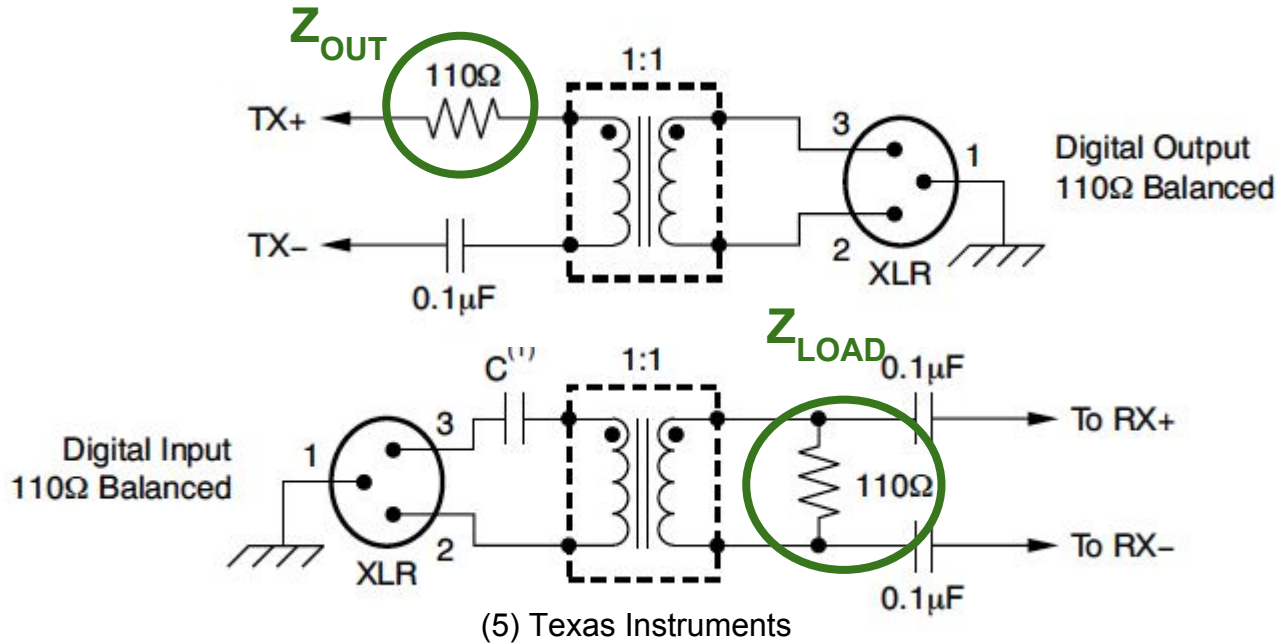


- AES/EBU inputs and outputs are designed for a 110-ohm transmission line, so use 110-ohm cable!

Review

- Voltage Transfer (Impedance Bridging)
 - Analog audio interfaces
 - Z_{in} should be $\sim 10 \times Z_{out}$ impedance
 - Keep reactance low, review cable capacitance for long cable runs
- Power Transfer (Impedance matching)
 - Matched Z_{in} and Z_{out} impedance maximizes power transfer
 - Typically necessary when the output is not low impedance
- Transmission Lines (Impedance Matching)
 - Matching Z_{in} and Z_{out} to the line impedance (Z_0) minimizes reflections
 - Minimizing reflections maintains signal integrity

Questions

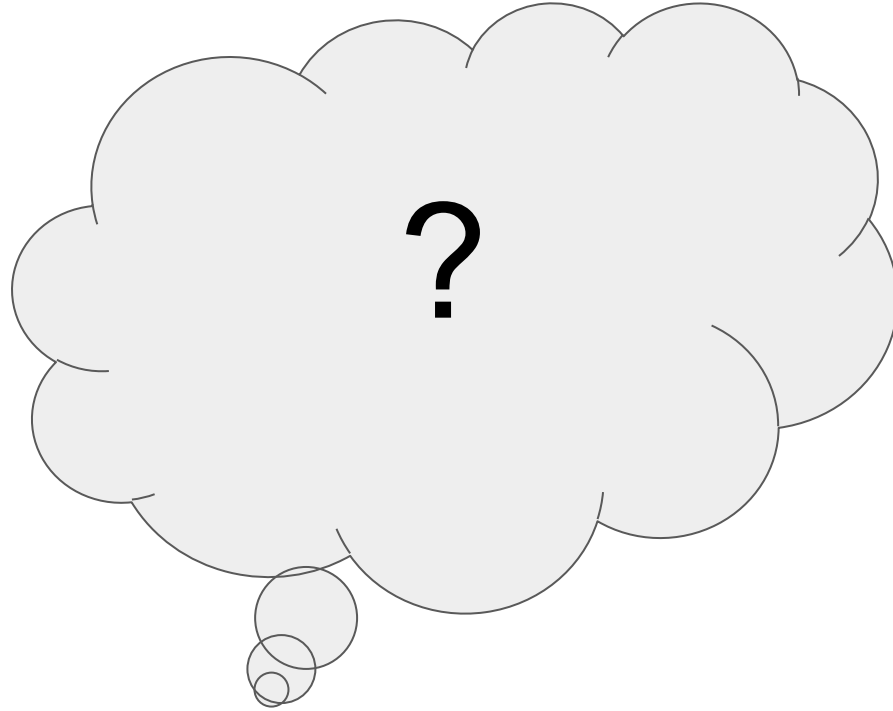

References

1. Bohn, Dennis. "Practical Line-Driving Current Requirements."
<http://www.rane.com/note126.html>. 1991 [Revised May 1996]. Web. 11 March 2017
2. Snow, William B. "Impedance -- Matched or Optimum?" *Journal of the AES*. Day Month Year. Web. March 11 2017
3. Ott, Henry. "Balanced vs. Unbalanced Audio Interconnections." *hottconsultants.com*. 2 July 2008. Web. 18 March 2017.
4. Whitlock, Bill and Rod Elliot. "Design of High-Performance Balanced Audio Interfaces"
<http://sound.whsites.net/articles/balanced-2.htm#s2>. 2010. Web. March 12 2017.
5. Texas Instruments. "DIX4192 Integrated Digital Audio Interface Receiver and Transmitter." DIX4192 datasheet. February 2006 [Revised September 2010].
6. FunScienceDemos. "Sound Light Travel in Waves" Youtube. Fun Science Demos. 14 March 2015.